


CSE436 Digital Integrated Circuits

Assignment 3 – Report



Ersel Celal Eren

1901042673

I have designed 2x1 inverting mux and then combined 3 of them to get 4x1 Mux. After designed the layout, I realized that at 1st version of my design when $S0 = 0$ and $S1 = 1$, mux selects D2 instead of D1 and when $S0 = 1$ and $S1 = 0$, mux selects D1 instead of D2. Then I replaced the labels of D2 and D1 in Magic layout and I get the following structure. Now this design is correctly working as it should.

 


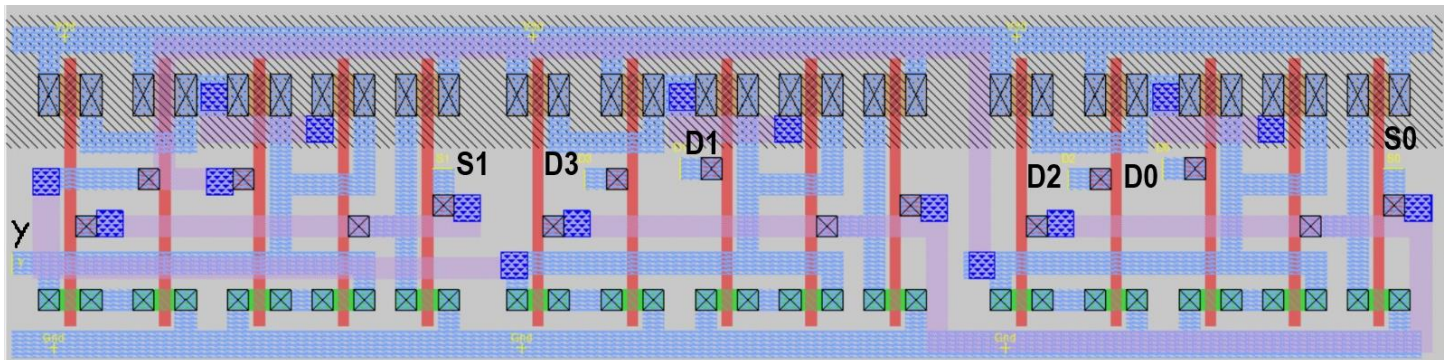 Here the following is Magic layout of 4x1 Mux using 3 2x1 Mux.




=====

First 2x1 Mux

 


=====

Second 2x1 Mux

 


=====

Third 2x1 Mux

 


Functionality Tests

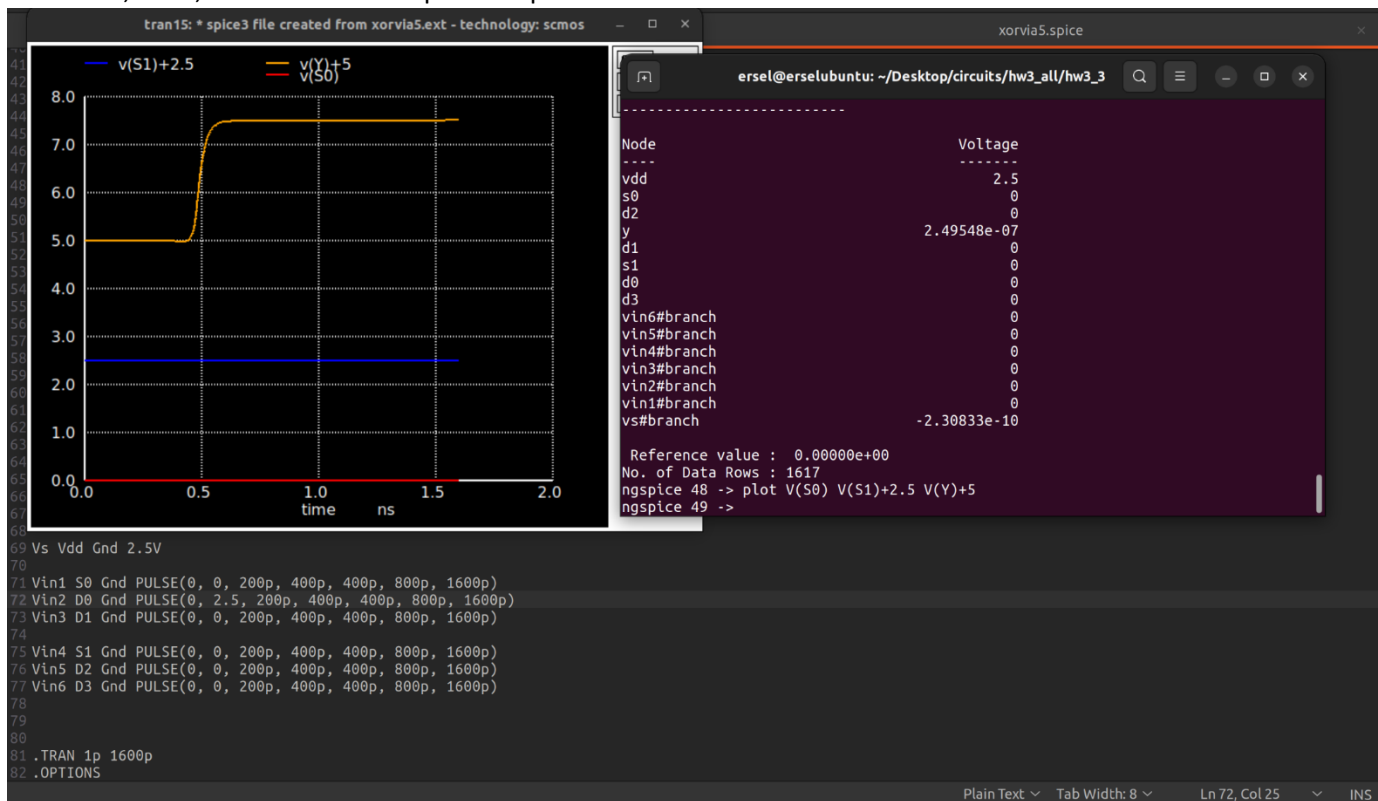
For $S_0 = 0, S_1 = 0$, mux selects D0 input as expected.



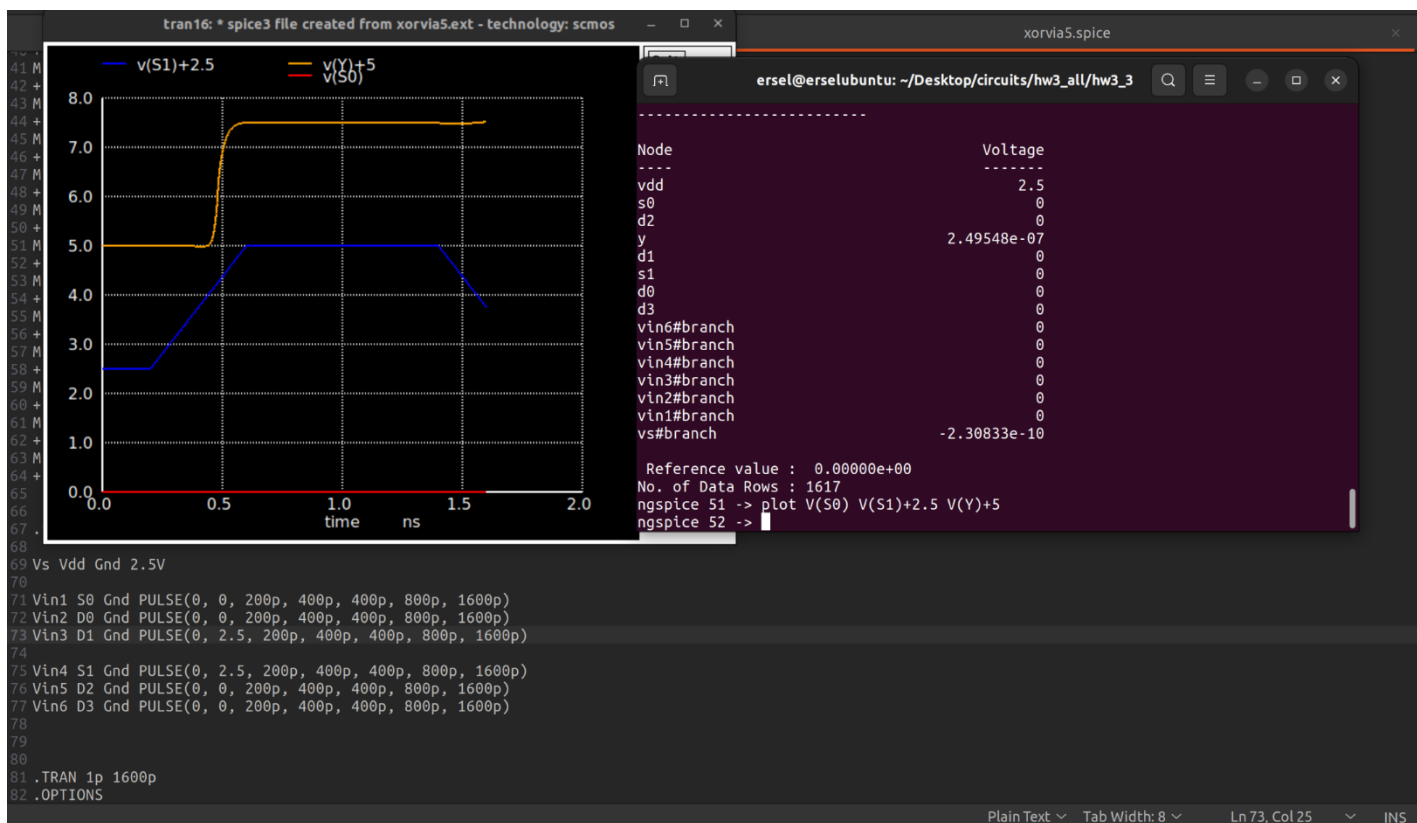
For $S_0=0$ and $S_1=1$, mux selects D1 input as expected.



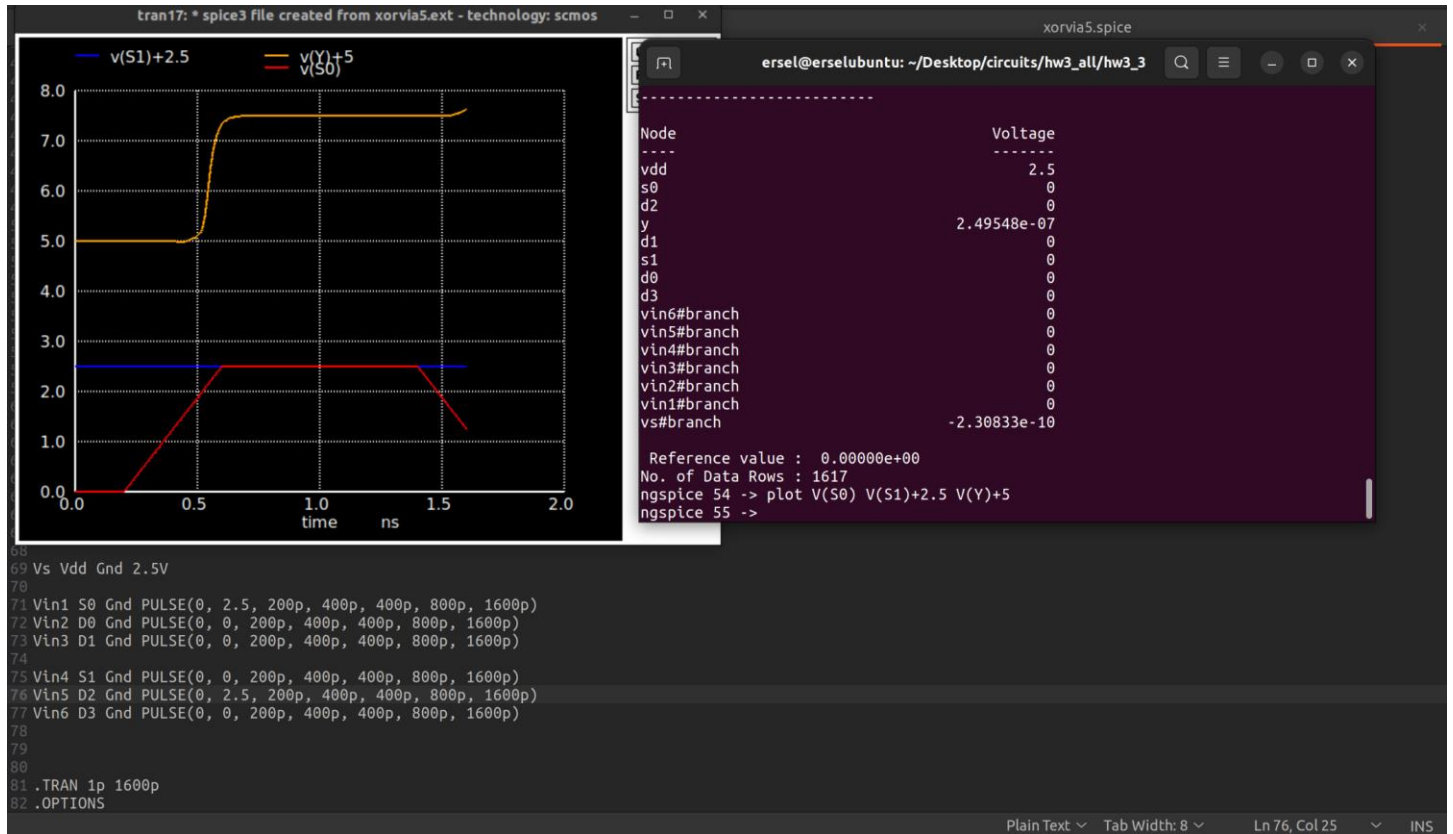For $S0 = 1$ and $S1 = 0$, mux selects D2 input as expected.



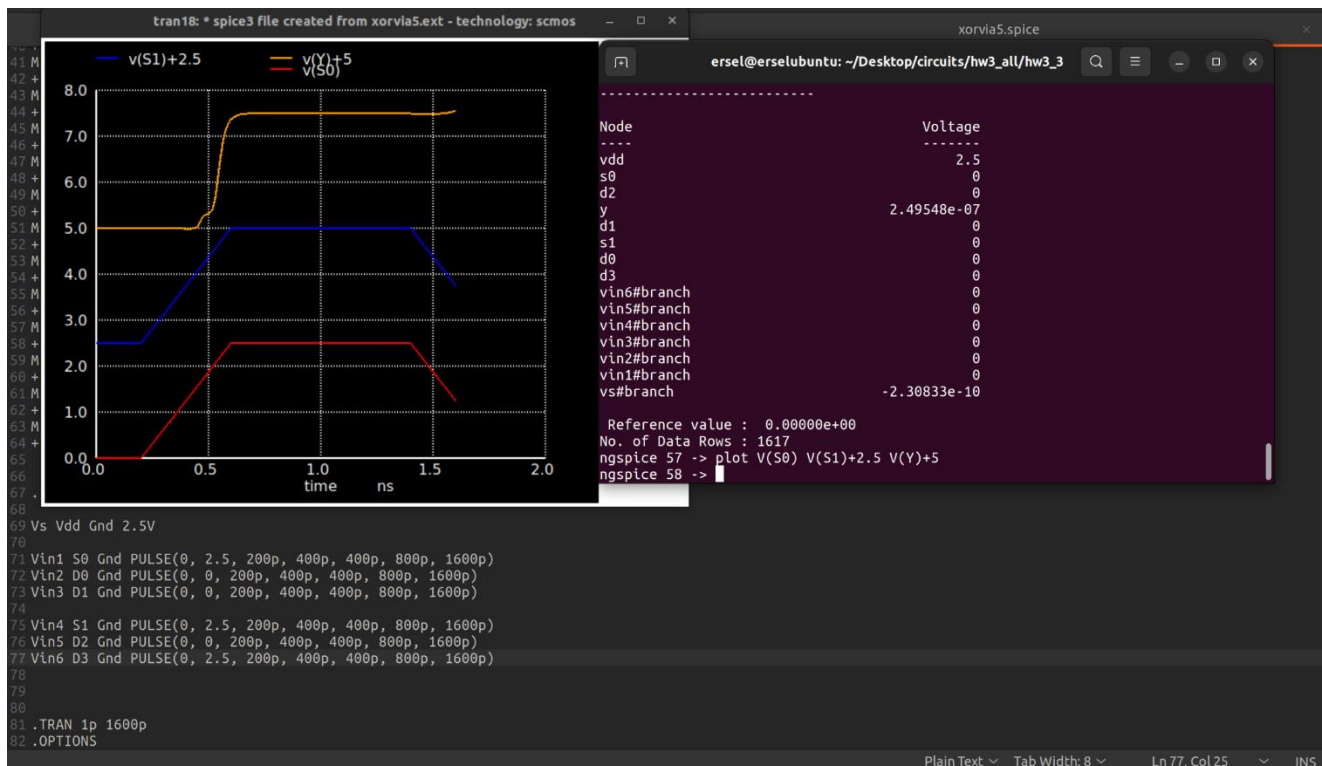For $S0 = 1$ and $S1 = 1$, mux selects D3 input as expected.




Critical Path Delay

I though occurs when

$S0 = 1 \mid S1 = 1$

$D0 = 0 \mid D1 = 1 \mid D2 = 0 \mid D3 = 1$

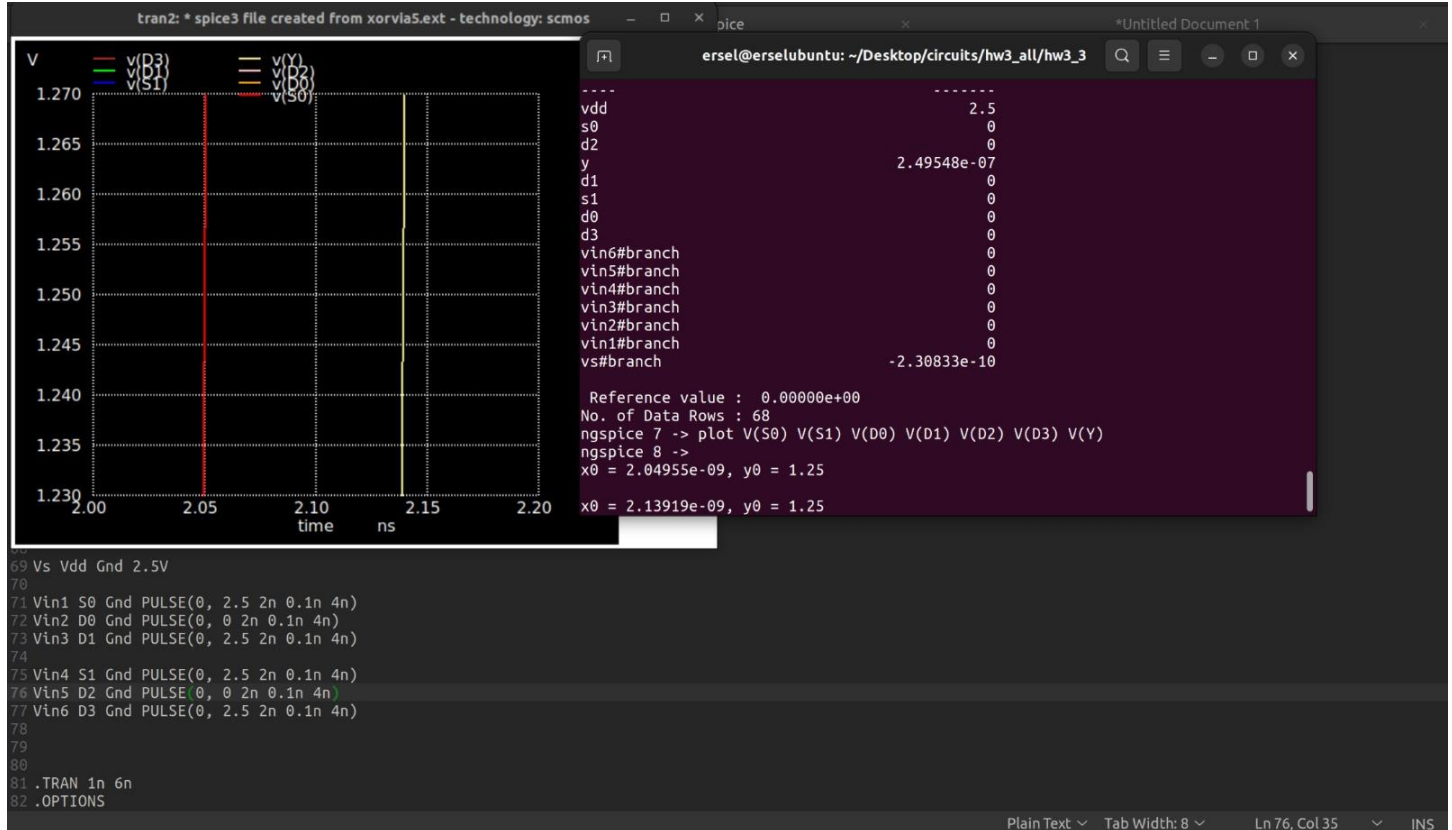Since in my design places of D1 and D2 are reversed, you may consider $D1 = 0$ and $D2 = 1$ in worst case.



Delay is 0.08964 nanoseconds.