


CSE 436 Digital Integrated Circuits


Ersel Celal Eren

1901042673


HW1 Report

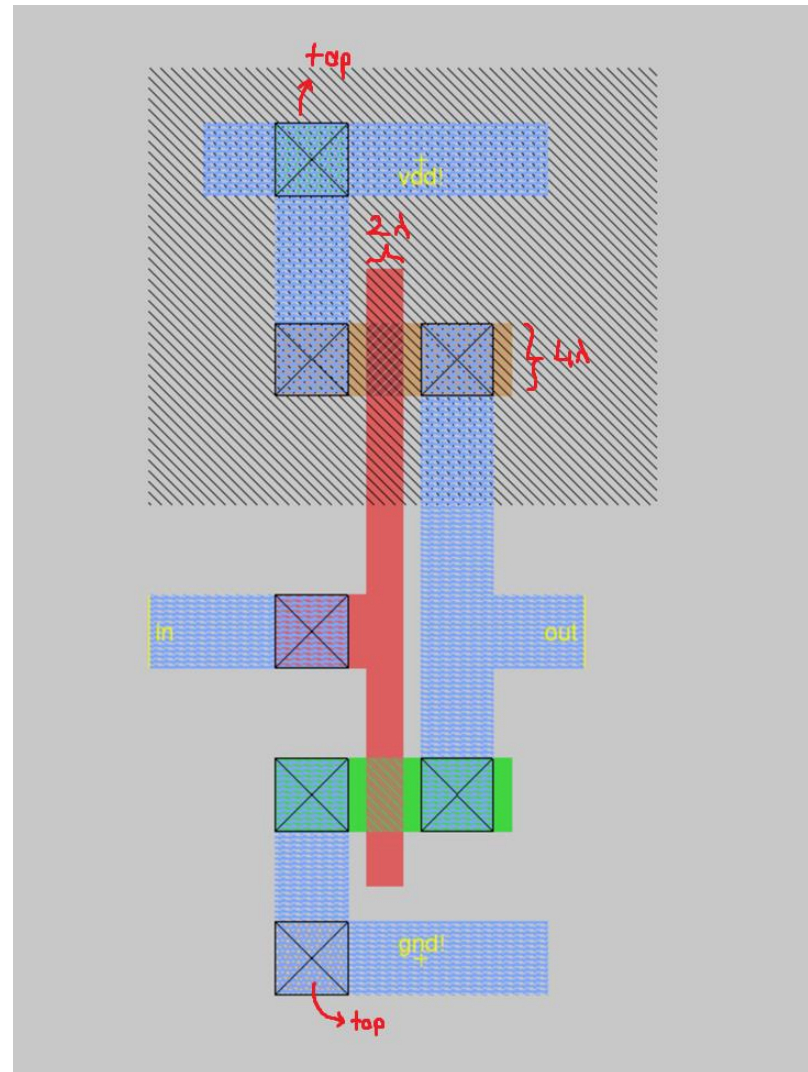This is the Magic Layout screenshot of inverter with $4\lambda/2\lambda$ PMOS and NMOS transistors and tap.




 

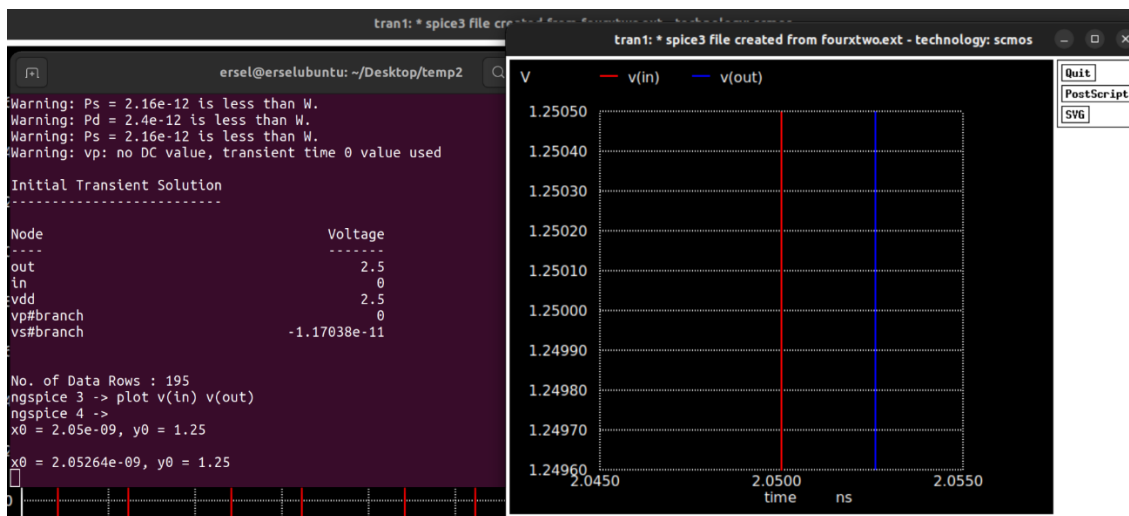This is the plotting of $v(in)$ and $v(out)$ for $4\lambda/2\lambda$ inverter.




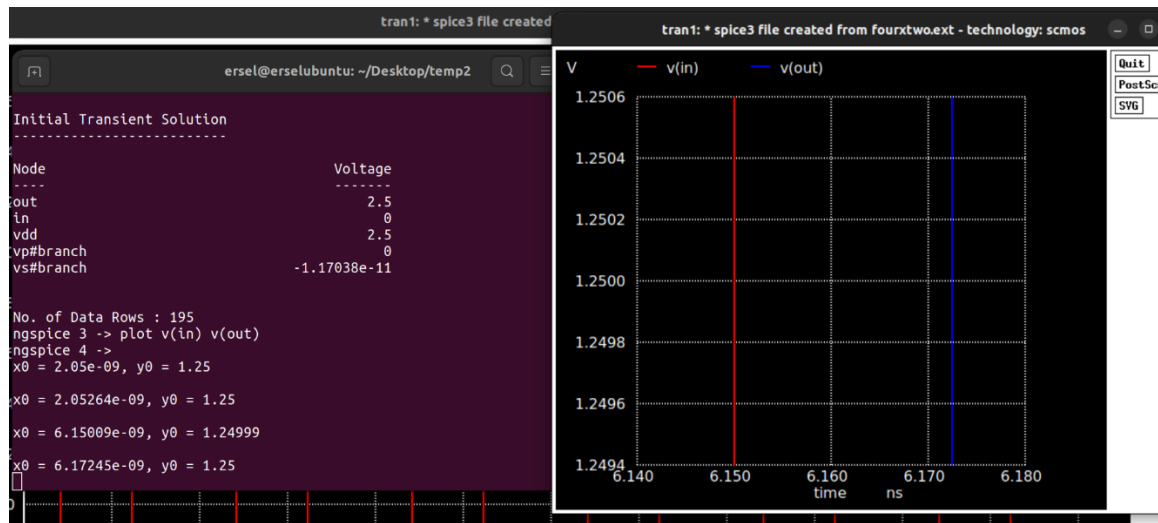
For the $4\lambda/2\lambda$ inverter, High-to-low delay, at 1.25 V(in) is $2.05e-09$, at 1.25 V(out) is $2.05264e-09$. So, the result is $2.64e-12$, which is 2.64 picoseconds.




For the $4\lambda/2\lambda$ inverter, Low-to-high delay, at 1.25 V(in) is 6.15009e-09, at 1.25 V(out) is 6.17245e-09. So, the result is 2.236e-08 seconds, which is 22.36 picoseconds.

 This is the Magic Layout
screenshot of inverter with
 $8\lambda/2\lambda$ PMOS and $4\lambda/2\lambda$ NMOS
transistors and tap.




 

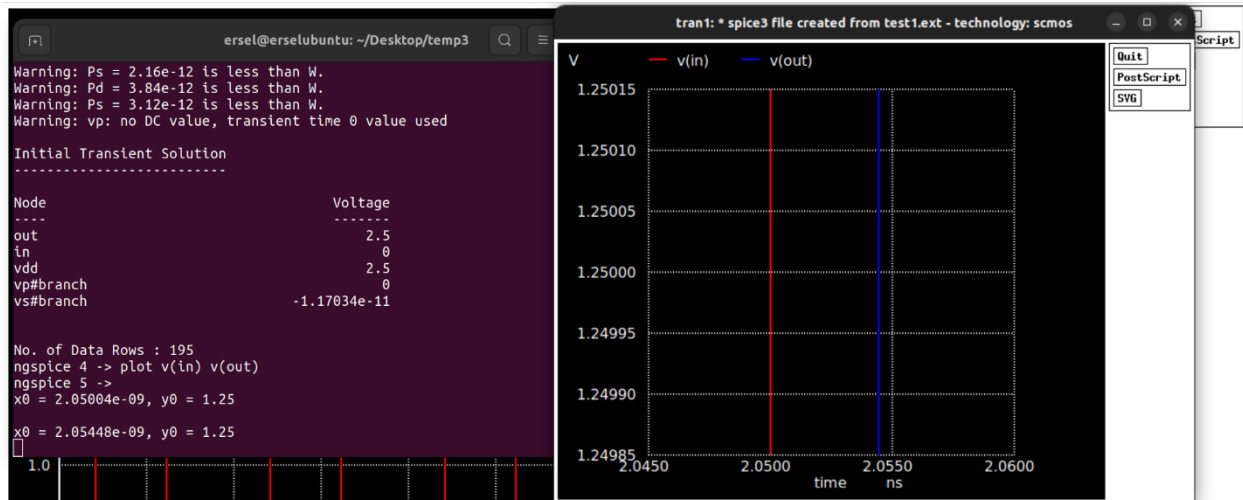This is the plotting of $v(\text{in})$ and $v(\text{out})$ for $8\lambda/2\lambda$ inverter.



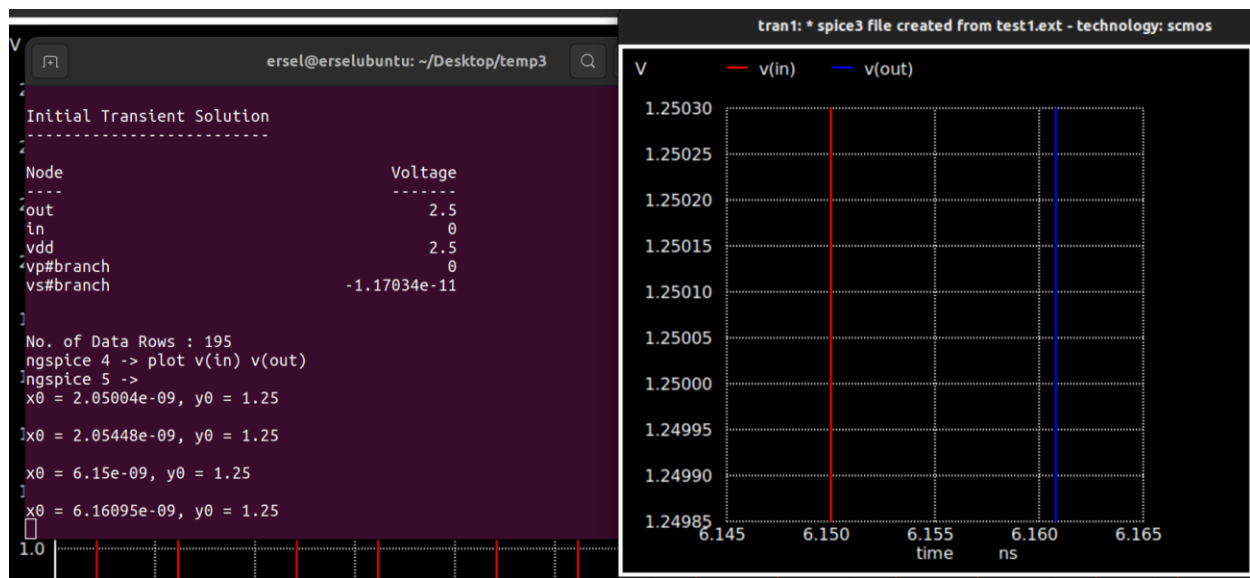For the $8\lambda/2\lambda$ inverter, High-to-low delay, at 1.25 V(in) is 2.05004e-09, at 1.25 V(out) is 2.05448e-09. So, the result is 4.44 picoseconds.



For the $8\lambda/2\lambda$ inverter, low-to-high delay, at 1.25 V(in) is 6.15e-09, at 1.25 V(out) is 6.16095e-09. So, the result is 10.95 picoseconds.

In low-to-high delay we can see that delay of $8\lambda/2\lambda$ inverter is smaller and in high-to-low delay is little bit bigger than $4\lambda/2\lambda$ inverter.

